Laborator Proiectare Logică 9

Sîrghe Matei


December 4, 2024

$$D: Q = D \nearrow$$
 - frontul ascendent


$$JK: \begin{cases} J \bigoplus K = 1; & Q = J \nearrow \\ J = K = 0; & Q = Q \nearrow \\ J = K = 1; & Q = \bar{Q} \nearrow \end{cases}$$


$$T: \begin{cases} T = 1; & Q = \bar{Q} \nearrow \\ T = 0; & Q = Q \nearrow \end{cases}$$

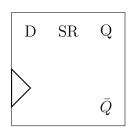Exerciții : $\begin{cases} D, +, Q_i = 1 & \text{SJDC} = 017028312031 \\ \text{BB - JR, -}, Q_i = 0 & \text{SJKC} = 15270E6E5201 \end{cases}$




#	S	R	D	С	Q	\bar{Q}
0	0	0	0	0	1	0
1	0	0	0	1	0	1
7	0	1	1	1	0	1
0	0	0	0	0	0	1
2	0	0	1	0	0	1
8	1	0	0	0	1	0
3	0	0	1	1	0	1
1	0	0	0	1	0	1
2	0	0	1	0	0	1
0	0	0	0	0	0	1
3	0	0	1	1	0	1
1	0	0	0	1	0	1

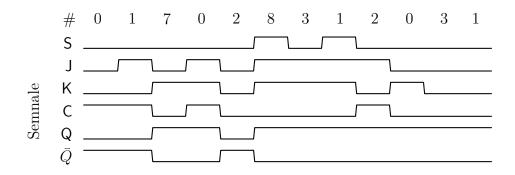

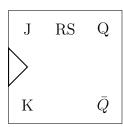


#	S	J	K	С	Q	\bar{Q}
1	0	0	0	1	0	1
5	0	1	0	1	0	1
2	0	0	1	0	1	0
7	0	1	1	1	1	0
0	0	0	0	0	0	1
E	1	0	1	0	1	0
6	0	1	1	0	1	0
E	1	1	1	0	1	0
5	0	1	0	1	1	0
2	0	0	1	0	1	0
0	0	0	0	0	1	0
1	0	0	0	1	1	0

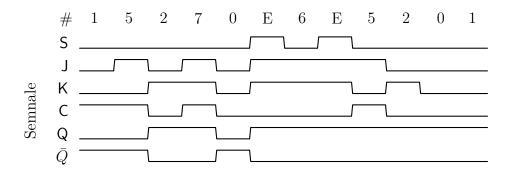

Exercițiul 3: $BBT; -; Q_o = 0, SRTC = 126912302030$

#	S	R	Т	С	Q	\bar{Q}
1	0	0	0	1	0	1
2	0	0	1	0	0	1
6	0	1	1	0	0	1
9	1	0	0	1	1	0
1	0	0	0	1	1	0
2	0	0	1	0	0	0
3	0	0	1	1	1	0
0	0	0	0	0	0	1
2	0	0	1	0	0	1
0	0	0	0	0	0	1
3	0	0	1	1	1	1
0	0	0	0	0	0	0

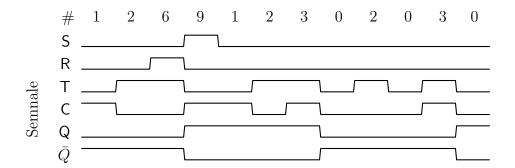

Exercițiul 4: $\begin{array}{c} {\rm BBB} & 0-2 \\ {\rm siner} & +-+ \\ D_0 = \bar{Q}_2 & J_1 = \bar{Q}_1 \\ K_1 = Q_2 & T_2 = Q_1 \end{array}$

